
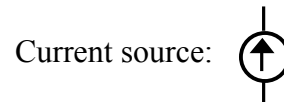



## P214 Midterm Practice Problems

(note that these are a little bit harder than the problems on the actual midterm will be, but are very good practice for them)

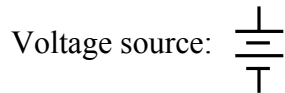
1. Show that, if you have a 15 volt battery, it is *not* possible to exceed the power rating of a  $\frac{1}{4}$  watt resistor of resistance greater than 1 k $\Omega$  (no matter how you connect it).
2. (A quite hard [especially parts b) – d]) but good problem!) Let's say that, instead of a voltage source (like a battery) or a constant-current source, we have a constant-power source. A constant-power source will do whatever it can to make sure that the voltage across its terminals, *multiplied by* the current it provides, is kept at a constant value (say, for example, 10 watts, or alternatively 100 milliwatts, etc). We know that the symbols for a voltage source and for a current source are as follows:



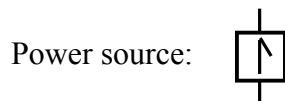
Let us let the symbol for a constant-power source be:



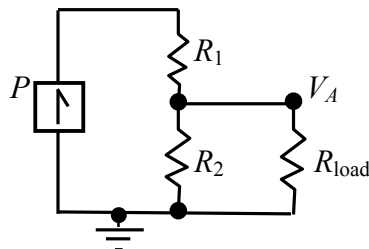And let's say we have the following circuit:




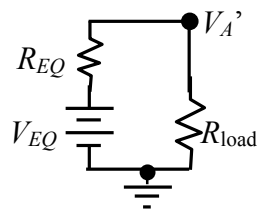- a) Find the voltage  $V_A$ , as a function of  $P$ ,  $R_1$ ,  $R_2$ , and  $R_{load}$ .
- b) If we decide to “formally” define the Thevenin equivalent voltage  $V_{EQ}$ , and Thevenin equivalent resistance  $R_{EQ}$ , as: 1)  $V_{EQ} \equiv V_A' = V_A$  in both of the circuits below and above respectively when taking the limit that  $R_{load} \rightarrow \infty$ , and 2)  $R_{EQ} \equiv R_{load}((V_{EQ}/V_A) - 1) = R_{load}((V_{EQ}/V_A') - 1)$  in both of the circuits above and below respectively when taking the limit that  $R_{load} \ll R_{EQ}$ , then find the Thevenin equivalents  $V_{EQ}$  and  $R_{EQ}$  as functions of  $P$ ,  $R_1$ , and  $R_2$ .



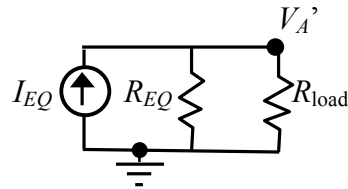
- c) If we decide to “formally” define the Norton equivalent current  $I_{EQ}$ , and Norton equivalent resistance  $R_{EQ}$ , as: 1)  $I_{EQ} \equiv V_A'/R_{load} = V_A/R_{load}$  in both of the circuits below and above respectively when taking the limit that  $R_{load} \ll R_{EQ}$ , and 2)  $R_{EQ} \equiv V_A/I_{EQ} =$

$V_A'/I_{EQ}$  in both of the circuits above and below respectively when taking the limit that  $R_{load} \rightarrow \infty$ , then find the Norton equivalents  $I_{EQ}$  and  $R_{EQ}$  as functions of  $P$ ,  $R_1$ , and  $R_2$ .



d) Does the Thevenin equivalent resistance  $R_{EQ}$  equal the Norton equivalent resistance  $R_{EQ}$  in your calculations above? Does  $V_{EQ} = I_{EQ}R_{EQ}$ , where  $R_{EQ}$  is the Thevenin equivalent resistance above?

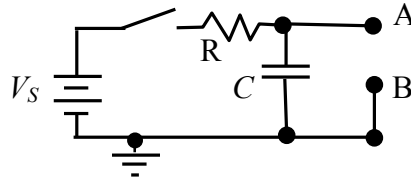3. At time  $t = 0$ , someone closes the switch of the circuit below. If we define the rise time of the circuit to be the time the circuit takes to go from 10% to 90% of its final value, show that the rise time of this circuit equals  $2.2RC$ .



4. Bugg problems 1.10.3, 1.10.6, 1.10.7, 1.10.9, 2.10.7, 2.10.8, 2.10.12, 2.10.13, 3.12.6, 3.12.13.