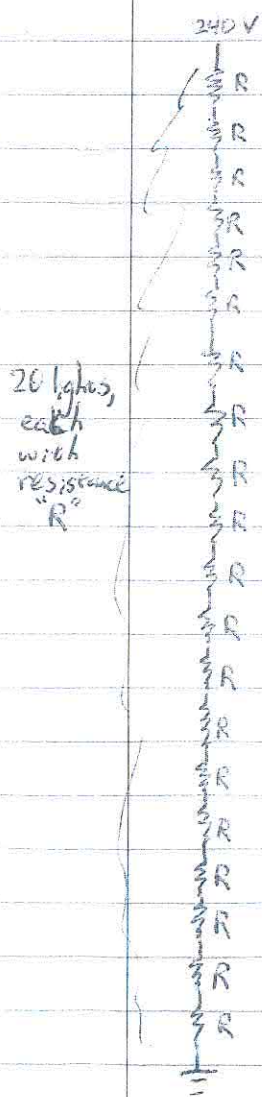


1.10.2 The x-mas lights:



are 20 bulbs connected in series, so their circuit diagram looks like this:



One of the bulbs "fuses," which we can interpret as it melting such that its resistance goes away and it effectively becomes a wire. Thus, after this fusing, we are in effect left with 19 bulbs in series (instead of 20)

The bulbs are "1 W bulbs," which we can interpret as meaning that before the fusing (when the lights are working as designed), each bulb dissipates 1 watt of power.

From that information, we can figure out the resistance R of each bulb: The voltage across each bulb (before the fusing) must equal $240/20$ volts = 12 volts. The power P dissipated in each bulb is given by $P = V^2/R$ (this is from $P = IV$ and $I = V/R$) = $12^2/R$. Thus, 1 watt = $\frac{144}{R}$, thus $R = 144 \Omega$.


Then, we can determine the current flow and power dissipation per bulb after the one bulb fuses. After the bulb fuses, there will be $\frac{240}{19} = 12.63$ V across each remaining bulb. The current flow will be $\frac{12.63 \text{ V}}{144 \Omega} = 87.72$ milliamps. And the power dissipated will be $\frac{12.63^2}{144} = 1.11$ watts. //

1.10.5

To find V_{xy} , note that the resistors with 330Ω and 220Ω resistance are in parallel, thus their combined resistance is $\frac{1}{\frac{1}{330} + \frac{1}{220}} = 132\Omega$. This is in series with the 100Ω resistor, so the circuit is acting like a "voltage divider" with $V_{xy} = 6 \times \frac{132}{100+132} = 3.41\text{ V}$. Then, we know that $V_{xy} = I_1 \times 330\Omega \Rightarrow I_1 = 10.34\text{ milliamps}$, and also that $V_{xy} = I_2 \times 220\Omega \Rightarrow I_2 = 15.51\text{ milliamps}$. //

1.10.8

(a) We have:

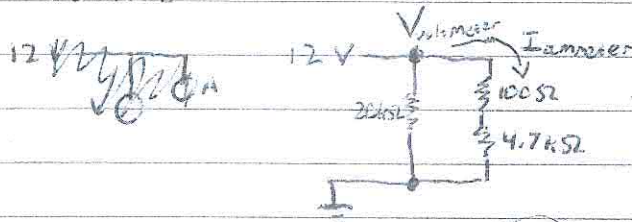


$V_{\text{voltmeter}}$ will clearly be 12 V in this case.

$$V_{\text{voltmeter}} = I_{\text{ammeter}} (100\Omega + 4700\Omega) \Rightarrow I_{\text{ammeter}} = \frac{12\text{ V}}{4800\Omega} =$$

$$2.5\text{ milliamps.}$$

(b) We have:

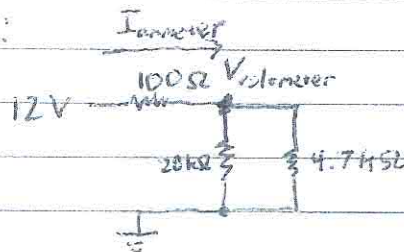


The $20\text{ k}\Omega$ and $4.7\text{ k}\Omega$ in parallel act like a $\frac{1}{\frac{1}{20} + \frac{1}{4.7}} = 3806\Omega$ resistor. Thus, this circuit acts like a "voltage divider" with

$$V_{\text{voltmeter}} = 12 \times \frac{3806}{3806+100} = 11.69\text{ V} \quad \text{and}$$

$$(12 - V_{\text{voltmeter}}) = I_{\text{ammeter}} \cdot 100\Omega \Rightarrow I_{\text{ammeter}} = \frac{0.31}{100} = 3.1\text{ milliamps.} //$$

Bugy 1.10.13

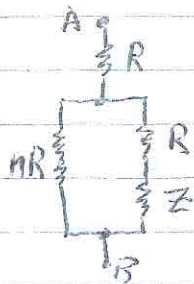Re-drawing the circuit shown, the first part of the question is equivalent to the question:



R_{eq} between points A and B equals Z . Find n in terms of R and Z .


Thus we have that $Z = R + \frac{1}{\frac{1}{nR} + \frac{1}{R+Z}} \Rightarrow \frac{1}{Z-R} = \frac{1}{nR} + \frac{1}{R+Z}$

$$\Rightarrow \frac{1}{nR} = \frac{1}{Z-R} - \frac{1}{Z+R} = \frac{Z+R}{Z^2-R^2} - \frac{Z-R}{Z^2-R^2} = \frac{2R}{Z^2-R^2}$$

$$\Rightarrow nR = \frac{Z^2-R^2}{2R} \Rightarrow n = \frac{Z^2-R^2}{2R^2} = 0.5 \left(\frac{Z^2}{R^2} - 1 \right) = \boxed{0.5(x^2-1)}$$

where $x = Z/R$.

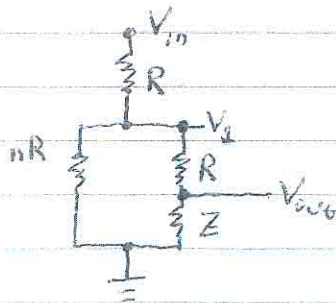To find the constant value A , we would like to find the voltage V_{out} in terms of V_{in} in this circuit:



To find V_{out} in terms of V_{in} , let us first find the voltage V_1 in terms of V_{in} . $V_1 = V_{in} \left(\frac{Z-R}{Z} \right)$. Now let's find V_{out} in terms of V_1 .




$V_{out} = V_1 \left(\frac{Z}{Z+R} \right)$. Now feeding the above equation in as shown,

$$V_{out} = V_{in} \left(\frac{Z-R}{Z} \right) \left(\frac{Z}{Z+R} \right) = V_{in} \left(\frac{Z-R}{Z+R} \right) = V_{in}/A$$

where $A = \frac{Z+R}{Z-R} = \frac{Z/R+1}{Z/R-1} = \frac{x+1}{x-1}$ where $x = Z/R$.

If $Z = 100\text{\$}$ and A is (a) 2, then $2 = \frac{x+1}{x-1} \Rightarrow Zx - 2 = x + 1$
 $\Rightarrow x = 3 \Rightarrow R = 33.35\%$ and $n = 4\%$ and if A is (b) 10, then
 $10 = \frac{x+1}{x-1} \Rightarrow 10x - 10 = x + 1 \Rightarrow 9x = 11 \Rightarrow x = \frac{11}{9} \Rightarrow$
 $R = \frac{900}{11}\% = 81.8\%$ and $n = 0.5\left(\frac{121}{81} - 1\right) = \frac{20}{81}\%$

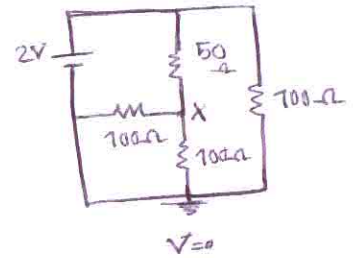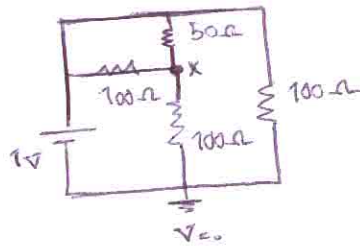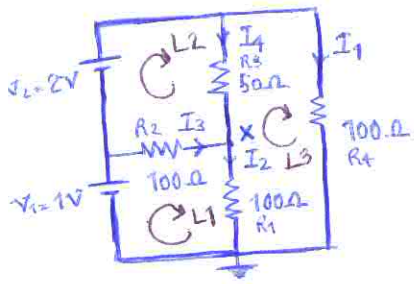If $A = 10$, then for example a 10% increase in R would
 drive A from 10 all the way up to 19 (a 90% increase in A),
 whereas if $A = 2$, then a 10% increase in R would only
 drive A from 2 to 2.16 (an 8% increase in A). So R needs to
 be much more stable in the case that $A = 10$ than when $A = 2$.



$$I = \frac{V}{R}$$

$$(I) \Rightarrow \frac{V_x}{100} + \frac{V_x - 1}{100} + \frac{V_x - 1}{50} = 0 \Rightarrow 4V_x = 3 \Rightarrow \boxed{V_x = \frac{3}{4} \text{ (V)}}$$

$$(II) \Rightarrow \frac{V_x}{100} + \frac{V_x}{100} + \frac{V_x - 2}{50} = 0 \Rightarrow 4V_x = 4 \Rightarrow \boxed{V_x = 1 \text{ (V)}}$$

$$\text{superposition principle} \Rightarrow V_x = 1 + \frac{3}{4} = \boxed{\frac{7}{4} \text{ (V)}}$$

$$I = \frac{V}{R} \Rightarrow$$

$$I_1 = \frac{3V}{100\Omega} = 30 \text{ mA}$$

$$I_3 = \frac{1V - 1.75V}{100\Omega} = -7.5 \text{ mA}$$

$$I_2 = \frac{1.75V}{100\Omega} = 17.5 \text{ mA}$$

$$I_4 = \frac{3V - 1.75V}{50\Omega} = 25 \text{ mA}$$

$$\left. \begin{aligned} L1: -V_1 + I_2 R_1 + I_3 R_2 &= 0 \\ L2: -V_2 - I_3 R_2 + I_4 R_3 &= 0 \\ L3: -I_2 R_1 + I_4 R_4 - I_4 R_3 &= 0 \end{aligned} \right\} \checkmark \leftarrow \text{check}$$

$$4) \quad Q = CV \Rightarrow Q = 2\mu F \times 12V = \underline{24\mu C}$$


$$E = \frac{1}{2} CV^2 = \frac{1}{2} \times 2\mu F \times (12)^2 V = \underline{144\mu J}$$

$$\# E = \frac{Q^2}{2C} = \underline{144\mu J}$$

$$5) \quad Q = \int_0^t I dt = CV$$


$$\Rightarrow V = \frac{1}{C} \int_0^{25} I dt = \frac{1}{C} \int_0^{25} (10t - 4t^2) dt = \frac{1}{10} \left(-\frac{4}{3} t^3 + 5t^2 \right) V$$

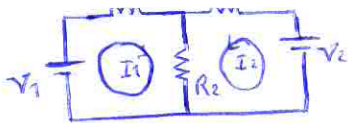... that $I \rightarrow \mu A$... $V \rightarrow V$



$$\star V_1 - I_1 R_1 - \left(\frac{R_2 R_3}{R_2 + R_3} \right) I_1 = 0$$
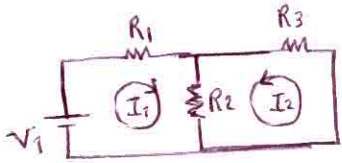
$$I_1 = \frac{V_1 (R_2 + R_3)}{\underbrace{R_1 R_2 + R_1 R_3 + R_2 R_3}_X} = \frac{V_1 (R_2 + R_3)}{X}$$




$$\Rightarrow V_1 - I_1 R_1 - (I_1 + I_2) R_2 = 0 \quad \star$$

$$\star \Rightarrow I_1 R_2 + I_2 R_2 = \frac{R_2 R_3}{R_2 + R_3} I_1 \Rightarrow I_1 \left(\frac{R_3}{R_2 + R_3} - 1 \right) = I_2$$

$$\frac{V_1 (R_2 + R_3)}{X} \left(\frac{R_3 - R_2 - R_3}{R_2 + R_3} \right) = I_2 \Rightarrow$$


$$\Rightarrow I_2 = - \frac{V_1 R_2}{X}$$

■ V_2 acting alone:

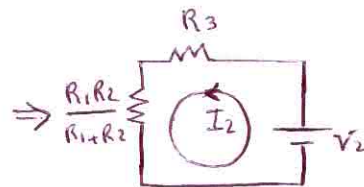

$$\star V_2 - I_2 R_3 - I_2 \left(\frac{R_1 R_2}{R_1 + R_2} \right) = 0$$
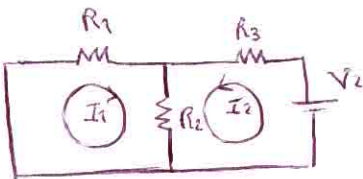
$$\Rightarrow I_2 = \frac{V_2 (R_1 + R_2)}{X}$$




$$\Rightarrow V_2 - I_2 R_3 - (I_1 + I_2) R_2 = 0 \Rightarrow$$

$$\star \star \Rightarrow (I_1 + I_2) R_2 = I_2 \left(\frac{R_1 R_2}{R_1 + R_2} \right)$$

$$I_1 R_2 + \frac{V_2 (R_1 + R_2) R_2}{X} = \frac{I_2 R_1 R_2}{R_1 + R_2}$$
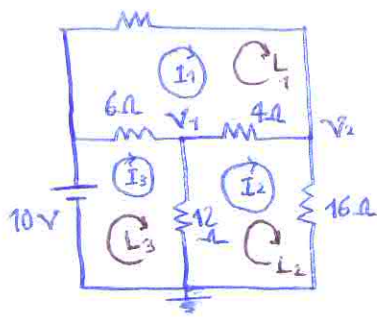
$$\Rightarrow I_1 = - \frac{V_2 R_2}{X}$$



$$I_{in} = I_{out} \quad , \quad I = \frac{V}{R}$$

$$\Rightarrow \left\{ \begin{array}{l} \text{for } V_1 \Rightarrow \frac{10 - V_1}{6} + \frac{V_2 - V_1}{4} = \frac{V_1}{12} \\ \text{for } V_2 \Rightarrow \frac{10 - V_2}{48} + \frac{V_1 - V_2}{4} = \frac{V_2}{16} \end{array} \right\} \Rightarrow \left\{ \begin{array}{l} \underline{V_1 = \frac{35}{6}} \\ \underline{V_2 = 5} \end{array} \right.$$

$$L_1 \Rightarrow 0 = 6(I_1 - I_3) + 48I_1 + 4(I_1 - I_2)$$

$$\underline{58I_1 - 4I_2 - 6I_3 = 0} \quad (I)$$

$$L_2 \Rightarrow 0 = 12(I_2 - I_3) + 4(I_2 - I_1) + 16I_2$$

$$\underline{32I_2 - 12I_3 - 4I_1 = 0} \quad (II)$$

$$L_3 \Rightarrow 10 = 6(I_3 - I_1) + 12(I_3 - I_2)$$

$$\underline{18I_3 - 6I_1 - 12I_2 = 10} \quad (III)$$

$$(I), (II), (III) \Rightarrow \left\{ \begin{array}{l} I_1 = \frac{5}{48} \\ I_2 = \frac{5}{16} \\ I_3 = \frac{115}{144} \end{array} \right.$$

