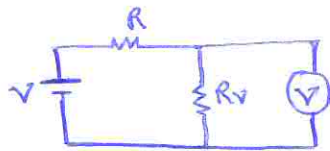


2.10.1)




case I) $V = (R + R_v)I_1 = RI_1 + R_v I_1$ & $R_v I_1 = 15 \Rightarrow I_1 = \underline{7.5 \times 10^{-4}}$

case II) $V = (R + R_v)I_2 = RI_2 + R_v I_2$ & $R_v I_2 = 18 \Rightarrow I_2 = \underline{3.6 \times 10^{-4}}$

$\Rightarrow (7.5 \times 10^{-4})R + 15 = (3.6 \times 10^{-4})R + 18 \Rightarrow \underline{R = 790 \Omega}$

$\underline{V = 20.8 \text{ V}}$

2.10.2)

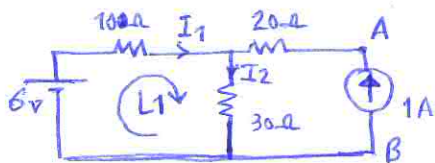


L1: $6 = 10I_1 + 30(I_1 + \underbrace{I_A}_{-1A}) \Rightarrow \underline{I_1 = -0.6 \text{ A}}$

$I_2 = I_A + I_1 = \underline{0.4 \text{ A}}$

$V_{AB} = I_A(20\Omega) + I_2(30\Omega) \Rightarrow \underline{V_{AB} = 32 \text{ V}}$

2.10.3)

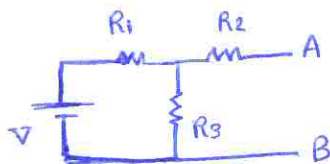


$V_{eq} = I_1 R_3$
 $I_1 = \frac{V}{R_1 + R_3}$ } $\Rightarrow \underline{V_{eq} = \frac{VR_3}{R_1 + R_3}}$

$R_{eq} = R_1 + \frac{1}{\frac{1}{R_2} + \frac{1}{R_3}} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2 + R_3}$

$I_{eq} = \frac{V_{eq}}{R_{eq}} = \frac{VR_3}{R_1 R_2 + R_2 R_3 + R_3 R_1}$

2.10.4)

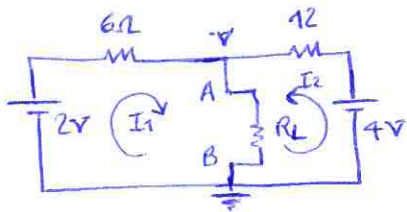


$$= \frac{V}{R} \left. \begin{array}{l} I_1 = \frac{2V}{6\Omega} = \frac{1}{3} A \\ I_2 = \frac{4V}{12\Omega} = \frac{1}{3} A \end{array} \right\} \Rightarrow I_{eq} = I_1 + I_2 = \frac{2}{3} A$$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2} = 4\Omega$$

$$V_{eq} = I_{eq} R_{eq} = \frac{8}{3} V$$

$$\left. \begin{array}{l} V_{AB} = I_{eq} R \\ R = \frac{R_L R_{eq}}{R_L + R_{eq}} \end{array} \right\} \Rightarrow V_{AB} = \frac{8 R_L}{3(4 + R_L)}$$


2.10.5)

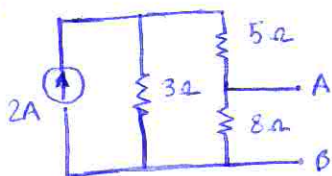


(a)




(b)

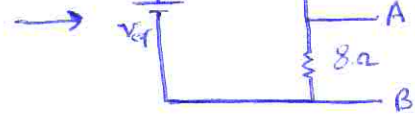


(c)

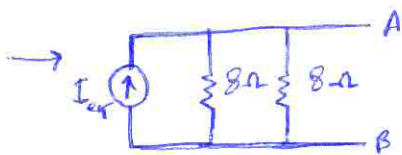

(d)

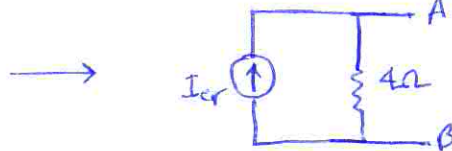

(e)

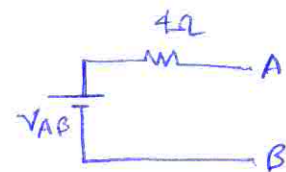

(f)

$$(a) \rightarrow (b) : V_{eq} = I_{eq} R_{eq} = (2A)(3\Omega) = 6V$$

$$(c) : \frac{V_{eq}}{16\Omega} = \frac{V_{AB}}{8\Omega} \rightarrow V_{AB} = 3V$$


$$R_{eq} = \frac{(8\Omega)(8\Omega)}{(8\Omega + 8\Omega)} = 4\Omega$$

$$I_{eq} = \frac{V_{eq}}{R_{eq}} = \frac{3V}{4\Omega} = 0.75A$$

2.10 6) a)
$$\begin{cases} 24 I_1 + 24(I_1 - I_2) = 0 \\ 24(I_2 - I_1) + 6(I_2 - I_3) = 0 \\ 2(I_3 + I_4) + 8I_3 + 6(I_3 - I_2) = 12 \\ 2(I_3 + I_4) + 8I_4 = 12 \end{cases}$$

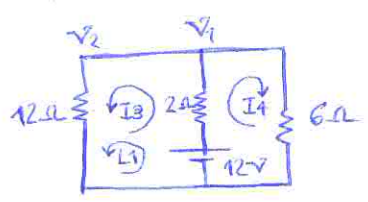b)
$$R_{eq} = 2\Omega + \frac{1}{\frac{1}{6\Omega} + \frac{1}{12\Omega}} = 6\Omega$$

$$I = \frac{V}{R_{eq}} = 2A = I_3 + I_4$$



c)
$$12V - V_1 = 2\Omega \times \underbrace{(I_3 + I_4)}_{2A} \Rightarrow \underline{V_1 = 8V}$$


L1:
$$12V = 2\Omega \times 2A + (12\Omega)(I_3) \Rightarrow \underline{I_3 = \frac{2}{3}A}$$

$$V_2 - V_1 = 8I_3 \Rightarrow \underline{V_2 = \frac{8}{3}V}$$

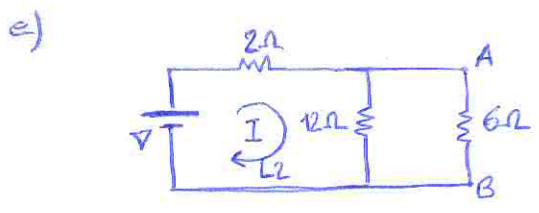d)
$$I_3 + I_4 = 2 \Rightarrow \underline{I_4 = \frac{4}{3}A}$$

$$V_2 = (I_3 - I_2)6\Omega \Rightarrow \frac{8}{3} = 4 - 6I_2 \Rightarrow \underline{I_2 = \frac{2}{9}A}$$


$$V_2 = I_1(24\Omega) \Rightarrow \underline{I_1 = \frac{1}{9}A}$$



$$\frac{1}{R_{eq}} = \frac{1}{12} + \frac{1}{6} \Rightarrow \underline{R_{eq} = \frac{24}{14}\Omega}$$

L2:
$$12 = 12I + 2I \Rightarrow \underline{I = \frac{12}{14}A} \Rightarrow V_{eq} = IR = \left(\frac{12}{14}\right)(12\Omega) = \underline{\frac{144}{14}V}$$


f)

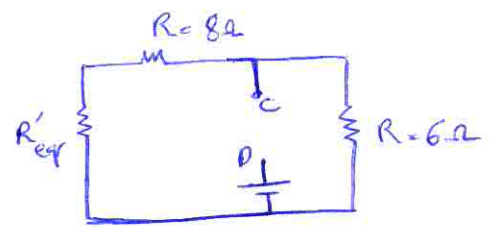

$$R'_{eq} = 4\Omega \quad , \quad R_N = \frac{1}{\frac{1}{R'_{eq} + 8\Omega} + \frac{1}{6\Omega}} \Rightarrow \underline{R_N = 4\Omega}$$

$$I_N = \frac{V}{R_N} = \frac{12V}{4\Omega} = \underline{3A}$$







g) chris' solution :

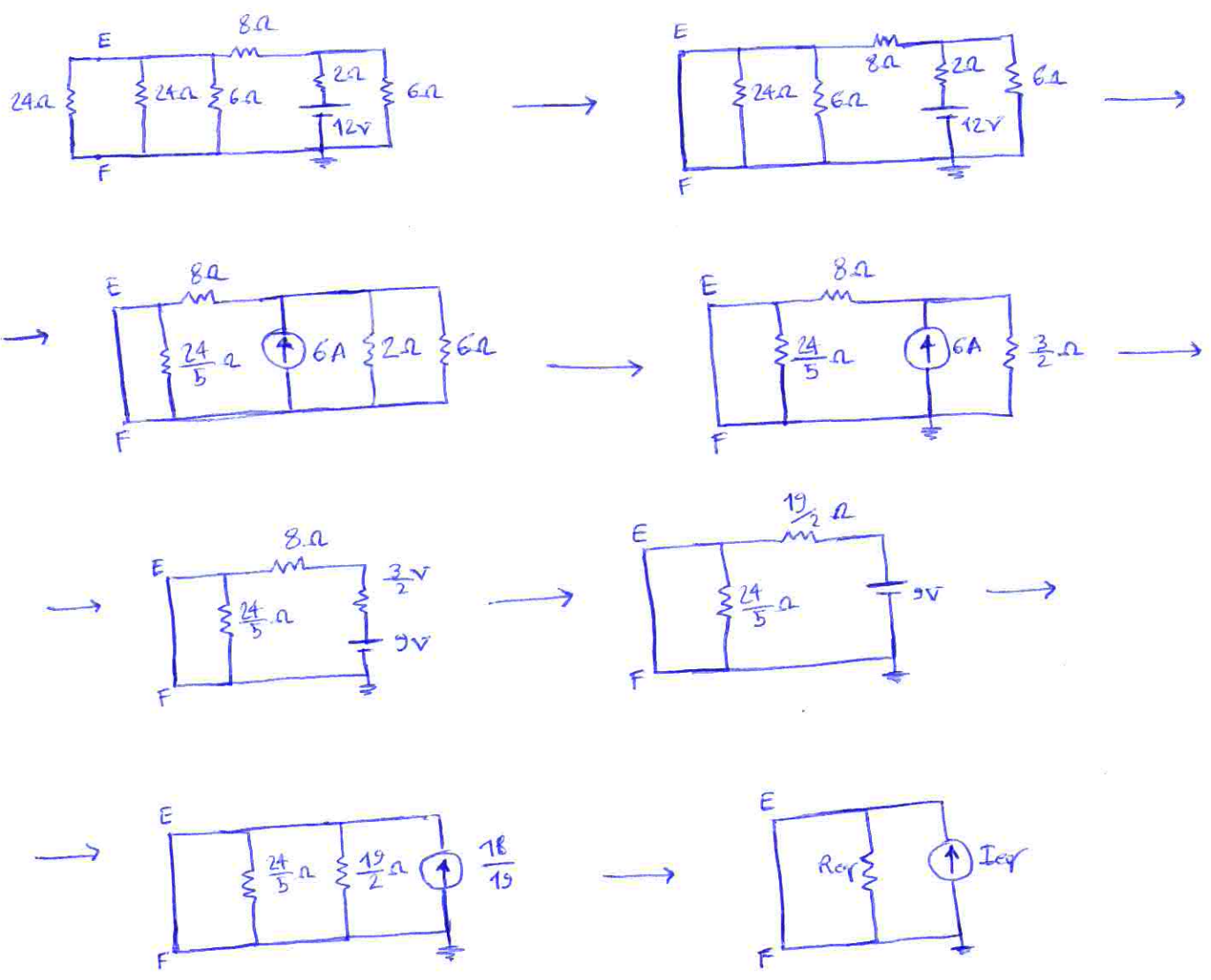


$$I_{eq} = I_N = \underline{\frac{18}{19} A}$$

$$R_{eq} = \frac{\frac{20}{5} \times \frac{19}{2}}{20 + 12} \Omega \rightarrow \underline{R_{eq} = \frac{456}{143} \Omega}$$

2.10.9)

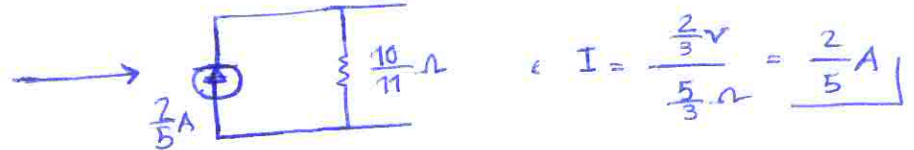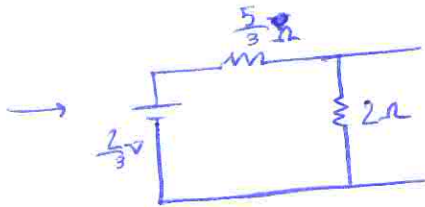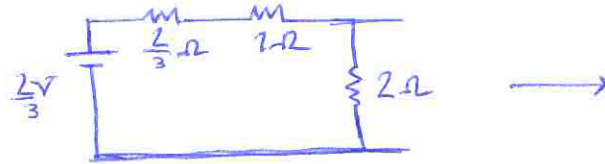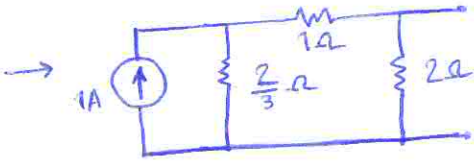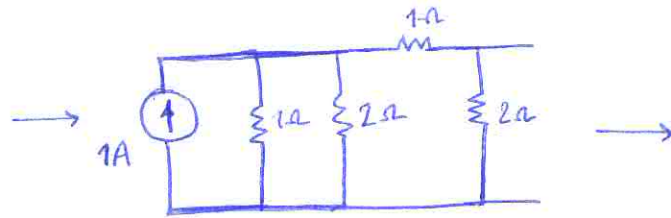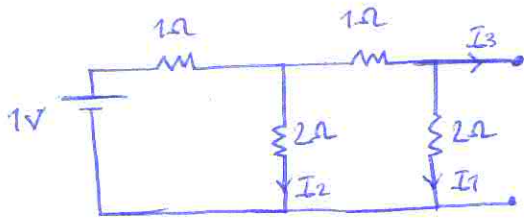


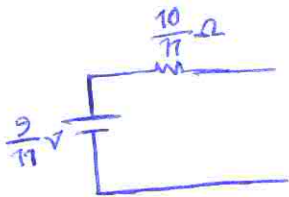
$$I = \frac{\frac{2}{3}V}{\frac{5}{3}\Omega} = \frac{2}{5}A$$



$$V = \left(\frac{2}{5}A\right) \left(\frac{10}{11}\Omega\right) = \frac{4}{11}V$$

$$R = \frac{1}{\frac{1}{5/3} + \frac{1}{2}} = \frac{10}{11}\Omega$$

2.10.10)

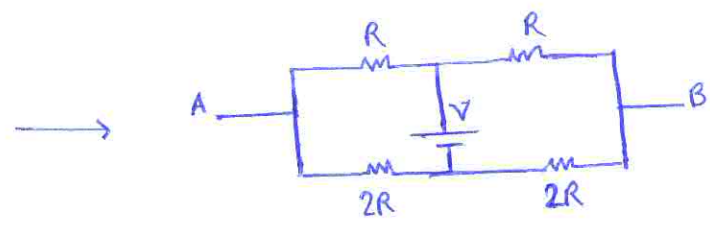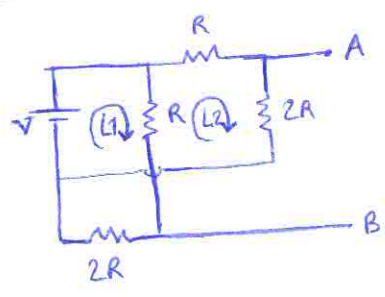

$$R_{eq} = \frac{1}{\frac{1}{R} + \frac{1}{2R}} + \frac{1}{\frac{1}{R} + \frac{1}{2R}} = \frac{4}{3}R$$

$$\left. \begin{aligned} L1: V - 3RI_1 &= 0 \\ L2: V - 3RI_2 &= 0 \end{aligned} \right\} \Rightarrow I_1 = I_2 = \frac{V}{3R}$$

$$V_{AB} = RI_2 - RI_1 = 0$$

3.12.7)

$$\left. \begin{aligned} V_R(t) + V_C(t) &= 12V \\ V_R(t) &= V_0 e^{-\frac{t}{RC}} \end{aligned} \right\} \Rightarrow \left. \begin{aligned} V_C(t) &= 12(1 - e^{-\frac{t}{RC}}) \\ R &= 1M\Omega \\ C &= 20\mu F \end{aligned} \right\} \Rightarrow$$

$$\Rightarrow V_C(t) = 12(1 - e^{-\frac{t}{20}})$$


3.12.8)

A : $V_A = V_0 e^{-\frac{t}{\tau}}$, $V_0 = 2V$, $\tau = RC$

after one time constant : $V_A = 2e^{-1} \approx 0.736V$

B : $V_B = V' e^{-\frac{(t-t_0)}{\tau}}$
 $V' = \underline{V_A - 3} \xrightarrow{-2.1} \Rightarrow \underline{V' = -2.264V}$
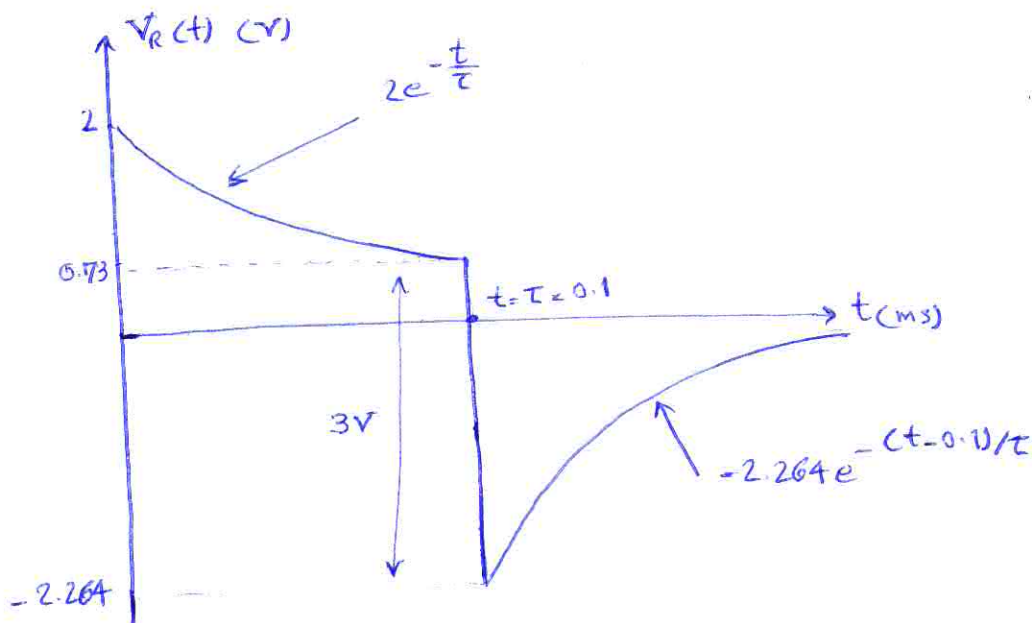
$$V_B = -2.264 e^{-\frac{(t-0.1)}{\tau}}$$



3.12.9)

$$V(t) = V(1 - e^{-\frac{t}{RC}})$$

$$, C = 20 \mu\text{F}$$

$$R = \frac{1}{\frac{1}{10 \text{ k}\Omega} + \frac{1}{22 \text{ k}\Omega}} = \underline{6.875 \text{ k}\Omega}$$

$$V = 6 - I(10 \text{ k}\Omega)$$

$$I = \frac{6 \text{ V}}{32 \text{ k}\Omega} = 187.5 \mu\text{A}$$

$$\Rightarrow \underline{V = 4.125 \text{ V}}$$

$$\Rightarrow \underline{V(t) = 4.125 (1 - e^{-\frac{t}{0.1375}})}$$

3.12.10)

$$I(t) = \frac{V_0 - V_R(t)}{R}$$

$$, V_0 = \frac{q}{C_1}$$

$$I(t) = \frac{V_0 - V_0 e^{-\frac{t}{RC'}}}{R}$$

$$, C' = \left(\frac{1}{C_1} + \frac{1}{C_2}\right)^{-1}$$

$$\Rightarrow \underline{I(t) = \frac{q}{RC_1} (1 - e^{-\frac{t}{RC'}})}$$

$$\Delta E = E_1 - E_2 = \frac{1}{2} \frac{q^2}{C_1} - \frac{1}{2} \frac{q^2}{C_1 + C_2}$$

$$\Rightarrow$$

$$\underline{\Delta E = \frac{1}{2} \frac{q^2 C_2}{C_1(C_1 + C_2)}}$$

