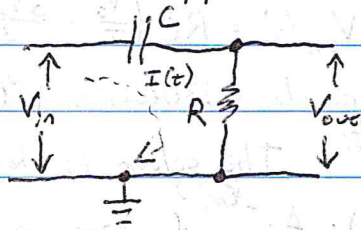


Physics 214 Problem Set #3 SOLUTIONS

Bugg problem #

3.12.11)

Let's consider the upper circuit first:



I have drawn in the current, and a ground, for reference. (There will be no current flow into V_{out} -- consider it to be like an oscilloscope.) From Ohm's Law, we have that

$$V_{out}(t) = I(t)R, \text{ and thus } I(t) = \frac{V_{out}(t)}{R}$$

From the capacitor relation $Q = CV$, we have that


$$Q(t) = C(V_{in}(t) - V_{out}(t)), \text{ and thus}$$

(differentiating this): $I(t) = C \left(\frac{dV_{in}(t)}{dt} - \frac{dV_{out}(t)}{dt} \right)$. We want to

find $V_{out}(t)$, so let's substitute $\frac{V_{out}(t)}{R}$ in for $I(t)$:

$$V_{out}(t) = RC \left(\frac{dV_{in}(t)}{dt} - \frac{dV_{out}(t)}{dt} \right) \quad (1)$$

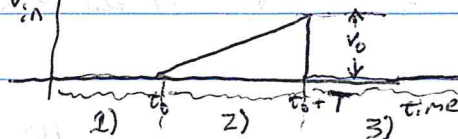This differential equation, (1), is the equation governing the behaviour of the above circuit. To go any further, we need to input the $V_{in}(t)$ that we are provided with, i.e. V_{in}



There are 3 parts to this waveform denoted by 1), 2), and 3) above.

Let's first consider part 1), where $\frac{dV_{in}(t)}{dt} = 0$, and the capacitor is initially uncharged. We have $V_{out}(t) = RC \left(\frac{dV_{in}(t)}{dt} - \frac{dV_{out}(t)}{dt} \right) = -RC \frac{dV_{out}(t)}{dt}$, thus

$$\int dt = -RC \int \frac{dV_{out}(t)}{V_{out}(t)} \Rightarrow \ln[V_{out}(t)] = -\frac{t}{RC} + (\text{constant of integration}) \Rightarrow$$

$$V_{out}(t) = Ae^{-t/RC}, \text{ where } A \text{ is a constant of integration.}$$

To find the constant A , we note that the initial condition is that the capacitor is uncharged, and thus $V_{out}(t)$ is initially zero, as is $V_{in}(t)$. Thus $A=0$, and thus, for part 1), $V_{out}(t)$ is just 0.

For part 2), $V_{in}(t)$ has a slope of $\frac{V_0}{T}$ (its rise over run), thus $\frac{dV_{in}(t)}{dt} = \frac{V_0}{T}$.

Thus (inputting this into equation ①): $V_{out}(t) = RC \left(\frac{V_0}{T} - \frac{dV_{out}(t)}{dt} \right)$. The way to solve that equation is to make the substitution $V'(t) \equiv V_{out}(t) - \frac{RCV_0}{T}$.


Then we have that $V'(t) = -RC \frac{dV'(t)}{dt}$. The solution to that differential equation (as for $V_{out}(t)$ in part 1) is $V'(t) = Ae^{-\frac{(t-t_0)}{RC}}$ for some constant A , and thus $V_{out}(t) = Ae^{-\frac{(t-t_0)}{RC}} + \frac{RCV_0}{T}$. We know that at time $t = t_0$, $V_{out}(t) = 0$, thus A must equal $-\frac{RCV_0}{T}$, and thus $V_{out}(t) = \frac{RCV_0}{T} \left(1 - e^{-\frac{(t-t_0)}{RC}} \right)$.

For part 3), we are back to the situation where $V_{in}(t) = 0$ and thus $V_{out}(t) = Ae^{-\frac{(t-t_0-T)}{RC}}$ for some constant A . To find A , we note that

the charge state of the capacitor cannot suffer a discontinuity (as having one would imply an infinite current), and thus $Q(t_0+T) = C(V_{in}(t_0+T) - V_{out}(t_0+T))$ must be the same right before and right after the end of the ramp. Right before the end of the ramp, we have that $Q(t_0+T) = C \left(V_0 - \frac{RCV_0}{T} \right) = CV_0 \left(1 - \frac{RC}{T} \right)$.


Right after the end of the ramp, we have that $Q(t_0+T) = C(-V_{out}(t_0+T)) = -CAe^{-\frac{(t-t_0-T)}{RC}} = -CA$. Thus $-CA = CV_0 \left(1 - \frac{RC}{T} \right) \Rightarrow A = -V_0 \left(1 - \frac{RC}{T} \right)$

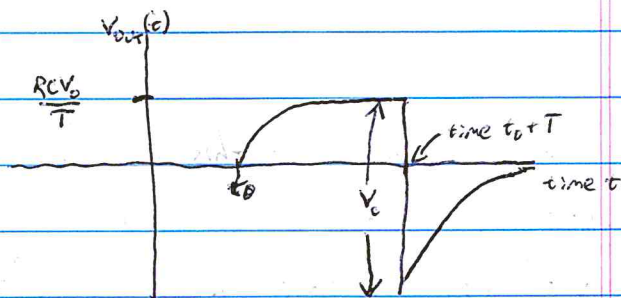$\Rightarrow V_{out}(t) = -V_0 \left(1 - \frac{RC}{T} \right) e^{-\frac{(t-t_0-T)}{RC}}$. The jump in $V_{out}(t)$ at $t = t_0+T$ is $-V_0 \left(1 - \frac{RC}{T} \right) - \frac{RCV_0}{T} = -V_0$. Plotted, this is



For the lower circuit, we have:

3.2.11 (cont'd)

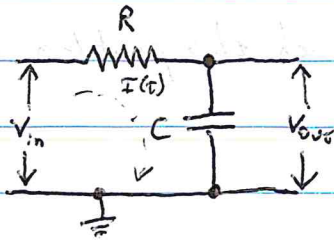

From Ohm's Law we have $V_{in}(t) - V_{out}(t) = I(t)R$, and from the capacitor relation we have $Q(t) = CV_{out}(t)$, and thus

$$I(t) = C \frac{dV_{out}(t)}{dt}$$

Thus we have that $\frac{V_{in}(t) - V_{out}(t)}{R} = C \frac{dV_{out}(t)}{dt}$, and thus

$$V_{out}(t) = V_{in}(t) - RC \frac{dV_{out}(t)}{dt}. \text{ Let's consider the}$$

3 parts of the input waveform again. In part 1), $V_{in}(t) = 0$, and thus

$$V_{out}(t) = -RC \frac{dV_{out}(t)}{dt}, \text{ thus } V_{out}(t) = Ae^{-t/RC} \text{ where } A \text{ is a constant of}$$

integration, and since both V_{in} and V_{out} are initially zero, $A=0$. For part

$$2), V_{in}(t) = \frac{V_0}{T}(t-t_0), \text{ thus } V_{out}(t) = \frac{V_0}{T}(t-t_0) - RC \frac{dV_{out}(t)}{dt}.$$

Make the substitution $V'(t) = V_{out}(t) - \frac{V_0}{T}(t-t_0) + \frac{RCV_0}{T}$. Then

$$V'(t) = -RC \frac{dV'(t)}{dt}, \text{ which implies } V'(t) = Ae^{-\frac{t-t_0}{RC}}, \text{ and thus}$$

$$V_{out}(t) = Ae^{-\frac{t-t_0}{RC}} + \frac{V_0}{T}(t-t_0) - \frac{RCV_0}{T}. \text{ We know that at } t=t_0,$$

$$V_{out}(t) = 0, \text{ thus } A = \frac{RCV_0}{T}, \text{ thus } V_{out}(t) = \frac{RCV_0}{T} \left(e^{-\frac{t-t_0}{RC}} - 1 \right) + \frac{V_0}{T}(t-t_0).$$

$$\text{We know that } e^{-\frac{t-t_0}{RC}} \approx 1 - \frac{t-t_0}{RC} + \frac{(t-t_0)^2}{2R^2C^2} - \dots \text{ (these are}$$

the first few terms of the Taylor series expansion for e^x), thus

$$V_{out}(t) \approx \frac{RCV_0}{T} \left(-\frac{t-t_0}{RC} + \frac{(t-t_0)^2}{2R^2C^2} \right) + \frac{V_0}{T}(t-t_0) = \frac{V_0(t-t_0)^2}{2TRC}. \text{ For part 3),}$$

$$\text{We are back to the situation where } V_{in}(t) = 0, \text{ and thus } V_{out}(t) = Ae^{-\frac{t-t_0-T}{RC}}$$


for some constant A . Again we note that the charge state of the capacitor

cannot suffer a discontinuity, and thus $Q(t) = CV_{out}(t)$ must be the same before


and right after the end of the ramp. Right before the end of the ramp,

$$V_{out}(t) \approx \frac{V_0 T}{2RC}, \text{ and thus after the ramp, it must have this same value, thus}$$

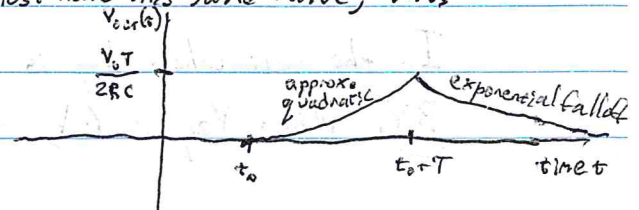
$$A = \frac{V_0 T}{2RC}, \text{ and thus } V_{out}(t) = \frac{V_0 T}{2RC} e^{-\frac{t-t_0-T}{RC}}.$$



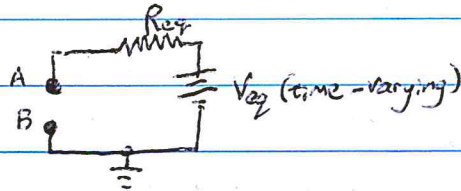3.12.12) I think the simplest way to approach this problem is to make a Thevenin equivalent circuit:



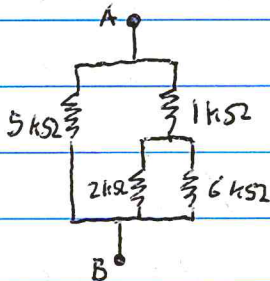To determine R_{eq} , we can redraw the circuit (with voltage sources changed to wires):




Thus $R_{eq} = \frac{1}{\frac{1}{5} + \frac{1}{1 + \frac{1}{\frac{1}{2} + \frac{1}{6}}}} \text{ k}\Omega = \frac{5}{3} \text{ k}\Omega$. The value of V_{eq} will

depend on whether we are inside a pulse, or outside of one. In any case, we can find V_{eq} via solving for current in current loops (when nothing is between A and B) -- we get the two equations


$24 - 8I_1 - 2I_2 = 0$ and $V_1 - 8I_1 - 2I_2 = 0$, where $V_1 = 6$ or 0 depending on whether we are in a pulse or not. We have $V_{eq} = 3I_1 + 2I_2 = 3(-0.8 + \frac{2V_1}{15}) + 2(3.2 - \frac{V_1}{30}) = 4 + \frac{V_1}{3}$, i.e. either 4 or 6 volts.

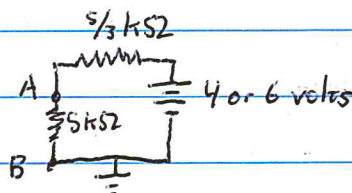(a) When a $5 \text{ k}\Omega$ resistor is connected between A and B, we have the equivalent circuit:



In the case where V_{eq} is 4V, the voltage at A will be $4 \times \frac{5}{20} =$
 $\textcircled{3V}$. When V_{eq} is 6V, the voltage at A will be $6 \times \frac{5}{30} = \textcircled{4.5V}$.

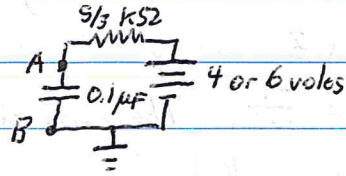3.2.12 (b) When a $0.1 \mu\text{F}$ capacitor is connected between A and B, we have the equivalent circuit:



We consider 3 parts of the input voltage "waveform": 1) V_{eq} is 4 volts and hasn't yet ever risen to 6 V, 2) V_{eq} enters a pulse and is thus 6V, and 3) V_{eq} falls back to 4V after a pulse. In all cases, we have Ohm's Law: $(V_{eq} - V_{AB}) = I \times \frac{5000}{3}$, and the capacitor relation

$$Q = V_{AB} \times 10^{-7} \Rightarrow I = 10^{-7} \frac{dV_{AB}}{dt}, \text{ and thus together they imply}$$

$$V_{eq} - V_{AB} = \frac{5 \times 10^{-4}}{3} \frac{dV_{AB}}{dt}. \text{ In parts 1) and 3), } V_{eq} = 4 \Rightarrow$$

$$4 - V_{AB} = \frac{5 \times 10^{-4}}{3} \frac{dV_{AB}}{dt}. \text{ Let } V' = V_{AB} - 4 \Rightarrow V' = -\frac{5 \times 10^{-4}}{3} \frac{dV'}{dt} \Rightarrow$$

$$V'(t) = Ae^{-\frac{3t}{5 \times 10^{-4}}} \Rightarrow V_{AB}(t) = 4 + Ae^{-\frac{3t}{5 \times 10^{-4}}}. \text{ For part 1),}$$

the V_{AB} is initially "charged up" to exactly 4 volts, so $A=0$. We

will go on to part 2) before solving for A in part 3). In part 2), $V_{eq} = 6 \Rightarrow$


$$6 - V_{AB} = \frac{5 \times 10^{-4}}{3} \frac{dV_{AB}}{dt} \Rightarrow V_{AB}(t) = 6 + Be^{-\frac{3(t-t_0)}{5 \times 10^{-4}}}. \text{ We know that at the}$$

$$\text{start of the pulse, } V_{AB}(t_0) = 4 \Rightarrow B = -2 \text{ and } V_{AB}(t) = 6 - 2e^{-\frac{3 \times 10^4 (t-t_0)}{5 \times 10^{-4}}}.$$

Now for part 3), $V_{AB}(t) = 4 + Ae^{-\frac{3(t-t_0-1\mu\text{s})}{5 \times 10^{-4}}}$, and we know that

$$V_{AB}(t_0 + 1\mu\text{s}) = 6, \text{ thus } A = 2 \text{ and } V_{AB}(t) = 4 + 2e^{-\frac{3 \times 10^4 (t-t_0-1\mu\text{s})}{5 \times 10^{-4}}}.$$

Plotting these out, we have

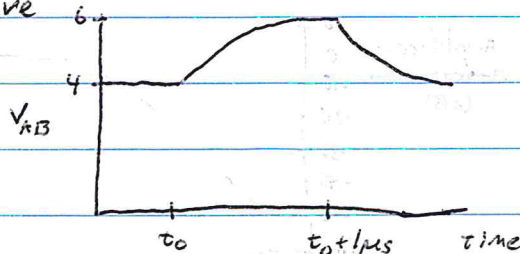

where the time constant $\tau = \frac{5 \times 10^{-4}}{3}$ seconds = 0.167 ms.


4.11.2) The impedance of a capacitor is given by the formula

$Z_{\text{capacitor}} = \frac{1}{i\omega C}$. (Z is the symbol for impedance, and ω is the angular frequency) $= \frac{-i}{\omega C}$. The norm of this imaginary number $\|\frac{-i}{\omega C}\|$ is $\frac{1}{\omega C}$, which is called the reactance. The impedance of

a $1 \mu\text{F}$ capacitance at (a) 50 Hz frequency, which corresponds to $\omega = 100\pi \frac{\text{rad}}{\text{s}}$ angular frequency, is thus $\frac{-i}{100\pi \times 10^{-6}} = \frac{-i}{\pi} \times 10^4 \text{ ohms}$,

and its reactance is $\frac{1}{\pi} \times 10^4 \text{ ohms}$. At (b) 10^6 Hz frequency, which corresponds to $\omega = 2\pi \times 10^6 \frac{\text{rad}}{\text{s}}$ angular frequency, the impedance is thus $\frac{-i}{2\pi \times 10^6 \times 10^{-6}} = \frac{-i}{2\pi} \text{ ohms}$ and its reactance is $\frac{1}{2\pi} \text{ ohms}$.


A high-pass RC filter has the form:

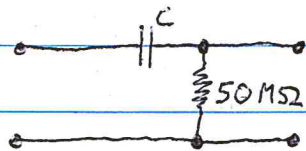

The capacitance C for a cutoff angular frequency $\omega = \frac{1}{RC} = 10^6 \frac{\text{rad}}{\text{s}}$

$\Rightarrow C = \frac{1}{50 \times 10^6 \times 10^6} = \frac{1}{50 \times 10^{12}} = 0.02 \text{ pF}$. The Bode plots plot

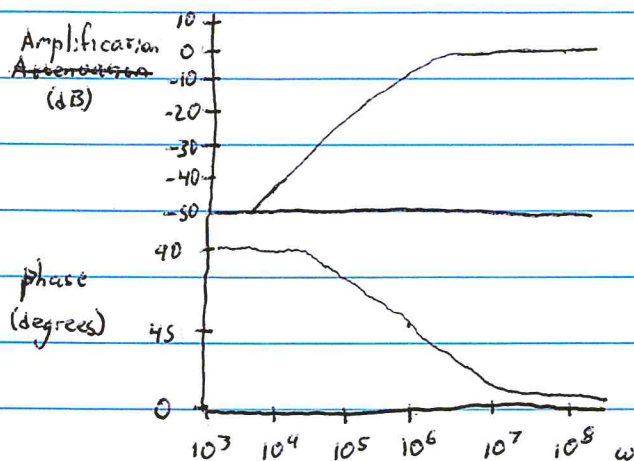the attenuation (in dB) and the phase shift, both as a function of the logarithm of the angular frequency ω . Thus the Bode plots will have the form




per figure 4.8 in the textbook.

4.11.5) (a) This is simply a voltage divider. To find $I(t)$, note that the total resistance is $80 \text{ k}\Omega$, and thus $I(t) = \frac{V(t)}{R} = \frac{3}{20} \cos(10^3 t)$ milliamps, the voltage across the $33 \text{ k}\Omega$ resistor is $V_{33 \text{ k}\Omega}(t) = \frac{99}{20} \cos(10^3 t)$ volts, and $V_{47 \text{ k}\Omega}(t) = \frac{141}{20} \cos(10^3 t)$ volts.

(b) This acts like a voltage divider as well. $Q(t) = CV(t) \Rightarrow I(t) = C \frac{dV(t)}{dt}$ with the total capacitance $C = \frac{1}{\frac{1}{1} + \frac{1}{3}} = 0.75 \mu\text{F}$. Thus $I(t) = -0.75 \times 10^{-6} \times 12 \omega \sin(\omega t) = -(9 \times 10^{-3}) \sin(10^3 t)$ amps ~~amps~~
 $= -9 \sin(10^3 t)$ milliamps. The voltage across the $1 \mu\text{F}$ capacitor will be $V_{1 \mu\text{F}}(t) = \frac{1}{1 \times 10^{-6}} \times \int I(t) dt = 9 \cos(10^3 t)$ volts, and the voltage across the $3 \mu\text{F}$ capacitor will be $V_{3 \mu\text{F}}(t) = \frac{1}{3 \times 10^{-6}} \times \int I(t) dt = 3 \cos(10^3 t)$ volts.

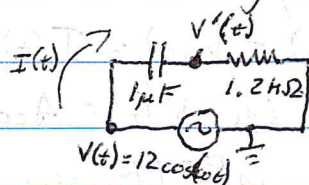(c) Call the voltage between the capacitor and the resistor $V'(t)$, and call the right-hand side of the voltage source ground as shown:



From Ohm's Law, we know $V'(t) = I(t) \times 1200$, and from the capacitor relation $Q = CV$, we know that $Q(t) = 10^{-6} \times (12 \cos(10^3 t) - V'(t))$ and thus $I(t) = 10^{-6} \times (-12000 \sin(10^3 t) - \frac{dV'(t)}{dt})$. Sub in $\frac{V'(t)}{1200}$ for $I(t)$ and we get $\frac{V'(t)}{1200} \times 1200$ for $V'(t)$ and we get

Eq. ①: $I(t) = -1.2 \times 10^{-3} \times (10 \sin(10^3 t) + \frac{dI(t)}{dt})$. To find the solution to that, assume that $I(t)$ is of the form $A \cos(10^3 t) + B \sin(10^3 t)$.

Substituting that into eq. ①, we have:

$$A \cos(10^3 t) + B \sin(10^3 t) = -1.2 \times 10^{-3} \times (10 \sin(10^3 t) - 10^3 A \sin(10^3 t) + 10^3 B \cos(10^3 t))$$

Collecting the coefficients in front of the cos terms and the sin terms separately:

$$\Rightarrow \begin{cases} A = -1.2B \\ B = 1.2A - 0.012 \end{cases}$$

The solution to those simultaneous equations is $A = 5.90 \times 10^{-3}$ and $B = -4.92 \times 10^{-3}$.

4.11.5 (c) Thus we have that $I(t) = (5.90 \cos(10^3 t) - 4.92 \sin(10^3 t))$ milliamps.

(cont'd)

This equals $C \cos(\omega t + \phi)$ milliamps, with $C = \sqrt{5.90^2 + 4.92^2} = 7.68$ and $\phi = \arctan\left(\frac{4.92}{5.90}\right) = 39.8^\circ$. The voltage $V'(t)$ across the resistor will equal $I(t)R = (1200 \times 7.68 \times 10^{-3}) \cos(\omega t + \phi)$ volts = $9.22 \cos(\omega t + 39.8^\circ)$ volts. The voltage across the capacitor will equal $12 \cos(\omega t) - 9.22 \cos(\omega t + 39.8^\circ) = 12 \cos(\omega t) - \frac{9.22 \times 5.90}{7.68} \cos(\omega t) + \frac{9.22 \times 4.92}{7.68} \sin(\omega t) = 4.92 \cos(\omega t) + 5.90 \sin(\omega t) = D \cos(\omega t + \eta)$ volts, with $D = \sqrt{4.92^2 + 5.90^2} = 7.68$ and $\eta = -\arctan\left(\frac{5.90}{4.92}\right) = -50.2^\circ$.

4.11.8) This problem is somewhat similar to 4.11.5(c) above. Call the voltage at the bottom of the circuit ground, and let $V(t)$ be the voltage between the resistor and the capacitor. Then $Q(t) = CV'(t) \Rightarrow I(t) = C \frac{dV'(t)}{dt}$ and $V \cos(\omega t) - V'(t) = I(t)R$, thus

$V \cos(\omega t) - V'(t) = RC \frac{dV'(t)}{dt}$. Let $V'(t) = A \cos(\omega t) + B \sin(\omega t) \Rightarrow V \cos(\omega t) - A \cos(\omega t) - B \sin(\omega t) = \omega RC (B \cos(\omega t) - A \sin(\omega t)) \Rightarrow$

$$V - A = \omega RCB \text{ and } -B = -\omega RCA \Rightarrow V - A = \omega^2 R^2 C^2 A \Rightarrow$$

$$A = \frac{V}{1 + \omega^2 R^2 C^2} \text{ and } B = \frac{\omega RCV}{1 + \omega^2 R^2 C^2}. \text{ The power dissipation in the circuit}$$

(which is all within the resistor) is $I^2(t)R$, and $I(t)$ will equal $\omega C (B \cos(\omega t) + A \sin(\omega t)) = \frac{\omega CV}{1 + \omega^2 R^2 C^2} (\omega RC \cos(\omega t) + \sin(\omega t))$. Thus

$$P(t) = \frac{\omega^2 C^2 V^2 R}{(1 + \omega^2 R^2 C^2)^2} (\omega^2 R^2 C^2 \cos^2(\omega t) + \sin^2(\omega t) + 2\omega RC \sin(\omega t) \cos(\omega t)).$$

To find the average power dissipation \bar{P} , we note that $\cos^2(x)$ and $\sin^2(x)$ both ~~over~~ always average out to $\frac{1}{2}$, and $\sin(x)\cos(x)$ averages to zero.

$$\text{Thus } \bar{P} = \frac{\omega^2 C^2 V^2 R}{2(1 + \omega^2 R^2 C^2)^2} (1 + \omega^2 R^2 C^2) = \frac{\omega^2 RC^2 V^2}{2(1 + \omega^2 R^2 C^2)} =$$

$$\frac{RV^2}{2(R^2 + (\frac{1}{\omega C})^2)}. \text{ This reaches a maximum when } \frac{d\bar{P}}{dR} = 0 \Rightarrow \frac{V^2}{2(R^2 + (\frac{1}{\omega C})^2)^2} - \frac{R^2 V^2}{(R^2 + (\frac{1}{\omega C})^2)^3} = 0$$


$$\Rightarrow \frac{V^2}{2(R^2 + (\frac{1}{\omega C})^2)^2} (1 - \frac{2R^2}{R^2 + (\frac{1}{\omega C})^2}) = 0 \Rightarrow 2R^2 = R^2 + (\frac{1}{\omega C})^2 \Rightarrow$$

$$R = \frac{1}{\omega C}. \bar{P} \text{ will have the same value if } R = \frac{1}{\omega C} + \alpha \text{ and}$$

$R = \frac{1}{\omega C} - \alpha$ for ^{very} small values of α . Setting $R = \frac{1}{\omega C}$ and putting

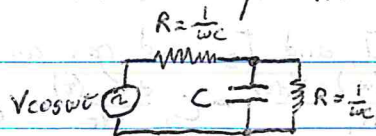4.11.8
(cont'd)

an equivalent resistance in parallel with C , we have the circuit



The Thevenin equivalent circuit across C :



has $R_{eq} = \frac{1}{2\omega C}$ and $V_{eq} = \frac{V}{2}$. Thus the current $I(t)$ will equal
 (from ①) $\frac{\omega C V}{2(1 + \omega^2 R_{eq}^2 C^2)} (\omega R_{eq} C \cos(\omega t) + \sin(\omega t)) = \frac{\omega C V}{5} (\cos(\omega t) + 2 \sin(\omega t))$
 $= \alpha \omega C V \cos(\omega t + \phi)$ for $\alpha = \sqrt{(\frac{1}{5})^2 + (\frac{2}{5})^2} = \sqrt{\frac{5}{25}} = \frac{1}{5}$ and
 $\phi = \arctan(2) = 63.4^\circ$, thus $I(t) = (\frac{\omega C V}{5}) \cos(\omega t + 63.4^\circ)$.

4.11.9)

The decibel scale is a logarithmic scale used to describe the ratio of two values of a quantity, which is often (but certainly not always!) power or intensity. Quantity Q , in decibels, with reference to a reference value Q_0 , is given by $dB_Q \equiv 10 \log_{10}(\frac{Q}{Q_0}) dB$.

This is 10 times its value in the (little-used) bel scale, $B_Q = \log_{10}(\frac{Q}{Q_0}) B$, hence decibel. Power in decibels can be expressed in terms of

voltage ratios because $\frac{1}{2}$ the power P dissipated in a resistor equals V^2/R , thus $dB_P \equiv 10 \log_{10}(\frac{P}{P_0}) = 10 \log_{10}(\frac{V^2/R}{V_0^2/R}) = 20 \log_{10}(\frac{V}{V_0})$.

If we have a reduction in voltage by a factor of 20, we have

$dB_P = 20 \log_{10}(\frac{1}{20})$ amplification = $-26 dB_P$ amplification =
 $+26 dB$ attenuation.

4.11.10)

Consider two loop currents $I_1(t)$ and $I_2(t)$ in the left and right (middle) loops respectively, both going clockwise.

Then from Kirchhoff's loop law, we have that:

$$1) V_s \cos(\omega t) - R_1 I_1(t) = V_x(t), \quad 2) V_x(t) - V_{out}(t) = I_2(t) R_2,$$

4.11.10 3) $I_1(t) - I_2(t) = C_1 \frac{dV_x(t)}{dt}$, and 4) $I_2(t) = C_2 \frac{dV_{out}(t)}{dt}$. Combining

(cont'd)

i), 3), and 4), we can eliminate I_1 and I_2 and get an equation in

terms of V_{out} and V_x : $\frac{V_s \cos(\omega t) - V_x(t)}{R_1} - C_2 \frac{dV_{out}(t)}{dt} = C_1 \frac{dV_x(t)}{dt}$, and

combining 2) and 4) we can get V_x in terms of V_{out} :

$V_x(t) = R_2 C_2 \frac{dV_{out}(t)}{dt} + V_{out}(t)$. Thus we can get an equation purely

for V_{out} : $\frac{V_s}{R_1} \cos(\omega t) - \frac{R_2 C_2}{R_1} \frac{dV_{out}(t)}{dt} - \frac{1}{R_1} V_{out}(t) - C_2 \frac{dV_{out}(t)}{dt} =$

$C_1 R_2 C_2 \frac{d^2 V_{out}(t)}{dt^2} + C_1 \frac{dV_{out}(t)}{dt} \Rightarrow$

$$\textcircled{1} \quad C_1 R_2 C_2 \frac{d^2 V_{out}(t)}{dt^2} + \left(C_1 + C_2 \left(1 + \frac{R_2}{R_1} \right) \right) \frac{dV_{out}(t)}{dt} + \frac{1}{R_1} V_{out}(t) = \frac{V_s}{R_1} \cos(\omega t).$$

As usual, assume $V_{out}(t)$ is of the form $A \cos(\omega t) + B \sin(\omega t)$ and

solve for A and B . $\frac{dV_{out}(t)}{dt} = \omega B \cos(\omega t) - \omega A \sin(\omega t)$ and

$\frac{d^2 V_{out}(t)}{dt^2} = -\omega^2 A \cos(\omega t) - \omega^2 B \sin(\omega t)$, thus feeding these into the ^{equation}

$\textcircled{1}$, and equating the cos terms and the sin terms, we get the

two equations

$$\textcircled{2} \quad -C_1 R_2 C_2 \omega^2 A + \left(C_1 + C_2 \left(1 + \frac{R_2}{R_1} \right) \right) \omega B + \frac{1}{R_1} A = \frac{V_s}{R_1} \quad \text{and}$$

$$\textcircled{3} \quad -C_1 R_2 C_2 \omega^2 B - \left(C_1 + C_2 \left(1 + \frac{R_2}{R_1} \right) \right) \omega A + \frac{1}{R_1} B = 0.$$

From equation $\textcircled{3}$, we get that $A = \frac{\frac{1}{R_1} - C_1 R_2 C_2 \omega^2}{\left(C_1 + C_2 \left(1 + \frac{R_2}{R_1} \right) \right) \omega} B$. Inserting that

into equation $\textcircled{2}$, we get $\left[\frac{\left(\frac{1}{R_1} - C_1 R_2 C_2 \omega^2 \right)^2}{\left(C_1 + C_2 \left(1 + \frac{R_2}{R_1} \right) \right) \omega} + \left(C_1 + C_2 \left(1 + \frac{R_2}{R_1} \right) \right) \omega \right] B = \frac{V_s}{R_1}$.

For very large angular frequencies ω , this becomes

$$\frac{C_1^2 R_2^2 C_2^2 \omega^3}{C_1 + C_2 \left(1 + \frac{R_2}{R_1} \right)} B = \frac{V_s}{R_1}$$

For very large angular frequencies ω , equations $\textcircled{2}$ and $\textcircled{3}$ become

$$\textcircled{2'} \quad -C_1 R_2 C_2 \omega^2 A \approx \frac{V_s}{R_1} \Rightarrow A \approx -\frac{V_s}{\omega^2 R_1 R_2 C_2}$$

$$\textcircled{3'} \quad -C_1 R_2 C_2 \omega^2 B \approx 0 \Rightarrow B \approx 0.$$

Thus for large frequencies, $V_{out}(t) \approx -\frac{V_s}{\omega^2 R_1 R_2 C_2} \cos(\omega t)$, and thus

$$\frac{V_{out}(t)}{V_{in}(t)} \approx -\frac{1}{\omega^2 R_1 R_2 C_2}$$

5.9.2)

We know that $V = L \frac{dI}{dt} =$ (in this case) $0.1 \times \frac{d}{dt}(25 \cos(100t)) =$
 $0.1 \times (-2500 \sin(100t)) = \underline{-250 \sin(100t)}$ volts.

5.9.3)

Since all current must flow through both the resistance and the inductance, the inductance will appear in series with R . The effective cutoff frequency of the filter this will form is $\omega = \frac{R}{L} = 4 \times 10^7 \frac{\text{rad}}{\text{s}}$, and since current must flow through the inductor, the inductor will ~~it~~ inhibit the passing of high-frequency signals, and will thus form a low-pass filter which will ~~the~~ tend to reject ~~the~~ angular frequencies greater than $4 \times 10^7 \frac{\text{rad}}{\text{s}}$.

