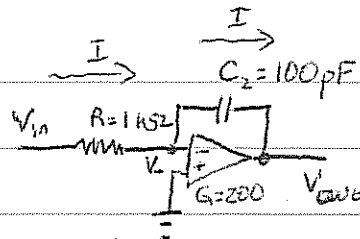


8.6.1(a) We have



and thus we have the 3 equations:

- 1) $V_{out} = -200V_-$ (gain of the amplifier)
- 2) $V_- - V_{in} = IR$ (Ohm's law)
- 3) $I = C_2 \left(\frac{dV_{out}}{dt} - \frac{dV_-}{dt} \right)$ ($Q = CV$)

Inserting 2) in 3), we get $V_- - V_{in} = RC_2 \left(\frac{dV_{out}}{dt} - \frac{dV_-}{dt} \right)$ and then replacing all V_- 's by $\frac{-V_{out}}{200}$ per 1), we have $V_{out} + 200V_{in} = -201RC_2 \frac{dV_{out}}{dt}$.
 Defining $V' \equiv V_{out} + 200V_{in}$, we have $V' = -201RC_2 \frac{dV'}{dt} \Rightarrow V' = Ae^{\frac{-t}{201RC_2}}$
 and thus $V_{out} = V' - 200V_{in} = Ae^{\frac{-t}{\tau}} - 200V_{in}$ where the time constant $\tau = 201RC_2 = 201 \times 1000 \times 10^{-10} = 2.01 \times 10^{-5}$ seconds.

(b) The easiest way to do this part is to use equation 8.11: the

bandwidth $\omega_c = \frac{\frac{1}{R_2} + \frac{1}{R_1(G+1)}}{C_2 + \frac{C_1}{G+1}}$. We have (initially) $R_2 = \infty$, $R_1 = 1000$, $G = 200$, $C_2 = 10^{-10}$ F, and $C_1 =$ (initially) 0.

Thus $\omega_c = \frac{\frac{1}{1000 \times 200}}{10^{-10}} = 5 \times 10^4 \frac{\text{rad}}{\text{s}}$.

If we add capacitor $C_1 = 10 \text{ pF} = 10^{-11} \text{ F}$ and resistor $R_2 = 10^4 \Omega$,


then the easiest way to find the amplification of the circuit at low frequency is to use the (un-numbered) equation at the bottom of p. 157, i.e. the amplification $\approx -\frac{R_2}{R_1} = -\frac{10000}{1000} = -10$.

To find the new bandwidth, we use equation 8.11 again: $\omega_c =$

$$\frac{\frac{1}{10^4} + \frac{1}{2.01 \times 10^4}}{10^{-10} + \frac{10^{-11}}{201}} \approx \frac{10^{10}}{10^9} = 10^6 \frac{\text{rad}}{\text{s}}$$

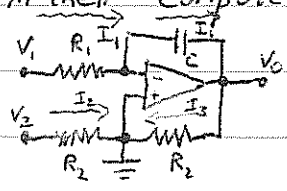8.6.2


First, let's demonstrate the relation given for the "Compute" setting: $V_{out} = -\int_0^t \frac{V_1 dt}{CR_1} - V_2$. Let's redraw the circuit when both switches are in their "Compute" $A=0, B=0$ setting:



We then have the following

- equations:
- 1) $V_1 = I_1 R_1$ (Ohm's law)
 - 2) $I_1 = -C \frac{dV_0}{dt}$ ($Q = CV$)
 - 3) $V_0 = I_2 R_2$ (Ohm's law)
 - 4) $V_2 = I_2 R_2$ (Ohm's law)

Combining 1) and 2), we have that $\frac{V_1}{R_1} = -C \frac{dV_0}{dt} \Rightarrow \frac{dV_0}{dt} = \frac{-V_1}{CR_1}$
 $\Rightarrow V_0 = -\int_0^t \frac{V_1 dt}{CR_1} + \text{constant}$, where the constant of integration is equal to the value of V_0 at time $t=0$. To determine what that value is, we need to know the initial condition. Let's take that initial condition to be the value V_0 takes after the circuit has been "Reset". The "Reset" ($A=1, B=1$) circuit is:

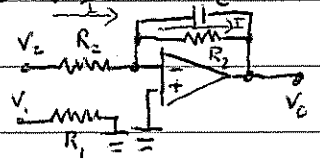


After sufficient time has passed, there will be no current flowing in the capacitor, and thus we have the two equations:

- 1') $V_2 = IR_2$
- 2') $-V_0 = IR_2$

and thus combining those equations we have $-V_0 = \frac{V_2 R_2}{R_2} \Rightarrow V_0 = -V_2$.

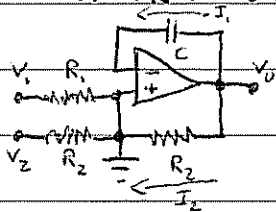We take this to be the initial condition to the "Compute" output, and thus, during "Compute," $V_0 = -\int_0^t \frac{V_1 dt}{CR_1} - V_2$, like the formula provided. As for the "Hold" setting, we then have:




giving the equations:

- 1'') $I_1 = C \frac{dV_0}{dt} = 0$
- 2'') $\frac{V_0}{R_2} = I_2 R_2$

etc.

Equation 1'') is the only one that matters for this setting. We have $\frac{dV_0}{dt} = 0$, and thus V_0 remains constant while the "Hold" setting remains in effect. Thus, each of the three settings do as they claim.

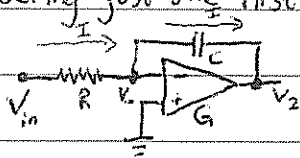8.6.3 i) Considering just the first half of the network, we have:



Since the gain of the amplifier is G , we have 3 equations:

$$1) V_2 = -GV_1 \quad (\text{gain of amp})$$

$$2) V_1 - V_2 = IR \quad (\text{Ohm's law})$$

$$3) I = C \left(\frac{dV_1}{dt} - \frac{dV_2}{dt} \right) \quad (Q=CV)$$

Combining 2) and 3), we have $V_1 - V_2 = RC \left(\frac{dV_1}{dt} - \frac{dV_2}{dt} \right)$. Then replacing all V 's with $\frac{-V_2}{G}$, per 1), we have

$$\frac{1}{CR} \left(\frac{V_2}{G} + V_1 \right) = - \left(1 + \frac{1}{G} \right) \frac{dV_2}{dt}$$

Swapping sides and integrating, we have $V_2 \left(1 + \frac{1}{G} \right) = - \frac{1}{CR} \int (V_1 + \frac{V_2}{G}) dt$.

ii) Neglecting terms of order $\frac{1}{G}$, the above is $V_2 = - \frac{1}{CR} \int V_1 dt$
 $= - \frac{1}{10^{-2} \cdot 10^6} \int 0.1 dt = -10 \times 0.1 t = -t$ volts. And $V_{out} \left(1 + \frac{1}{G} \right) =$

iii) Using the trial substitution mentioned, we have

$$(Ae^{\beta t} + B) \left(1 + \frac{1}{G} \right) = - \frac{1}{CRG} \int (Ae^{\beta t} + B + GV_1) dt$$

Performing the integral, we have $(Ae^{\beta t} + B) \left(1 + \frac{1}{G} \right) = - \frac{1}{CRG} \left[\frac{A}{\beta} e^{\beta t} + Bt + GV_1 t \right]_0^t \Rightarrow$
 $(Ae^{\beta t} + B) \left(1 + \frac{1}{G} \right) = \frac{A}{CRG\beta} (1 - e^{\beta t}) - \frac{t}{CRG} (B + GV_1)$. Now we need

to solve for $A, B,$ and β in terms of $C, R, G,$ and V_1 . Since the terms linear in t must cancel, B must equal $-GV_1$. We then know that

the constant terms must be equal and the exponential terms must also be equal, thus $B \left(1 + \frac{1}{G} \right) = \frac{A}{CRG\beta}$ and $A \left(1 + \frac{1}{G} \right) = - \frac{A}{CRG\beta}$. From the second of these equalities, $\beta = \frac{-1}{CR(G+1)}$, and from the first, $\frac{A}{CRG\beta} = -V_1(G+1)$

$$\Rightarrow A = -V_1 CRG\beta(G+1) = GV_1$$

iv) After $t=1$ second, V_1 returns to 0 volts, and we have that $V_2 \left(1 + \frac{1}{G} \right) = - \frac{1}{CR} \left(\int_0^1 \frac{V_1 dt}{G} + \int_1^t V_1 dt \right)$
 $= - \frac{1}{CR} \int_0^1 \frac{V_1 dt}{G} = - \frac{1}{10^{-2} \cdot 10^6} \int_0^1 0.1 dt = - \frac{1}{CR} \int_0^1 \frac{V_1 dt}{G} = -1$. Thus, ignoring terms of order $\frac{1}{G}$,

we have that V_2 settles down to ≈ -1 volt. $V_{out} \left(1 + \frac{1}{G} \right) \approx - \frac{1}{CR} \left(\int_0^t \frac{V_1 dt}{G} + \int_t^t V_2 dt \right) \approx$

ignoring terms of order $\frac{1}{G}$ $= \frac{1}{CR} \int_0^t -1 dt = 10t$ volts, and thus will grow linearly to saturation.

ii) $-\frac{1}{CR} \int (V_1 + \frac{V_2}{G}) dt =$ (ignoring terms of order $\frac{1}{G}$) $= - \frac{1}{CR} \int -t dt = -10 \left(-\frac{t^2}{2} \right) = 5t^2$ volts.

9.9.5 If the applied voltage is 250 V RMS, the peak applied voltage will be $250\sqrt{2} = 353.6$ V, thus the peak voltage across the output and load resistors will be $353.6 - 0.6 = 353$ V. The peak current will be $\frac{V}{R_{\text{total}}} = \frac{353}{1\text{k}\Omega + 200\Omega} = \frac{353}{1200} = 0.294$ A.

9.9.6 From the hyperphysics webpage (sent via e-mail), the peak-to-peak ripple will be $V_{r(\text{pp})} = \frac{V_{p(\text{in})} T}{R_L C}$, where T is the time between peaks. For 50 Hz input, T will be $\frac{1}{100}$ of a second, since there will be two positive peaks per cycle for full-wave rectified output as in this circuit. Thus, $V_{r(\text{pp})} = \frac{0.01 V_{p(\text{in})}}{R_L C}$. $V_{r(\text{pp})}$ will equal $V_{p(\text{in})} \left(1 - \frac{1}{20 R_L C}\right) = \left(1 - \frac{0.005}{R_L C}\right) V_{p(\text{in})}$. Thus, the magnitude of the ripple will equal as a fraction of the peak voltage will equal $V_{r(\text{pp})}/V_{p(\text{in})} = \frac{0.01}{R_L C}$, and we want to find the minimum value of R_L so that this is less than 5%. Thus, we have $0.05 = \frac{0.01}{R_L C}$. $C = 500 \mu\text{F} = 0.0005$ F, thus $0.05 = \frac{0.01}{0.0005 R_L} \Rightarrow 0.05 = \frac{20}{R_L} \Rightarrow R_L = 400 \Omega$. Note that this is different than the book's answer of 800Ω ; this is likely because Bugg was not accounting for the fact that 50 Hz ^{AC} input implies that the time between full-wave rectified peaks is $\frac{1}{100}$ second, not $\frac{1}{50}$ second. (If one uses the incorrect latter value, one gets the book's incorrect answer of 800Ω .) Given the correct answer of 400Ω , the DC current through the load will be approximately $\frac{250\sqrt{2}}{400} = 0.88$ A, twice the book's value of 0.44 A.